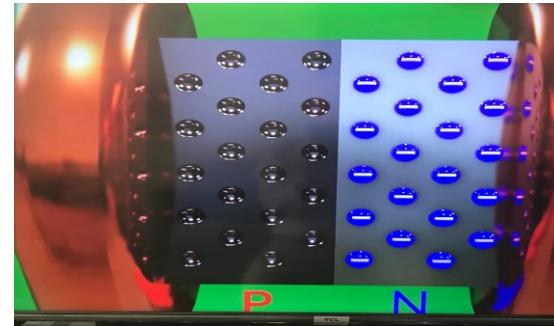







**P N MATERIAL
BETWEEN CONDUCTORS**





**Direct Polarization
Causes Electrons to Flow
With Voltage
Light is Emitted**



**P N IS OFFSET
TO INCREASE LIGHT**

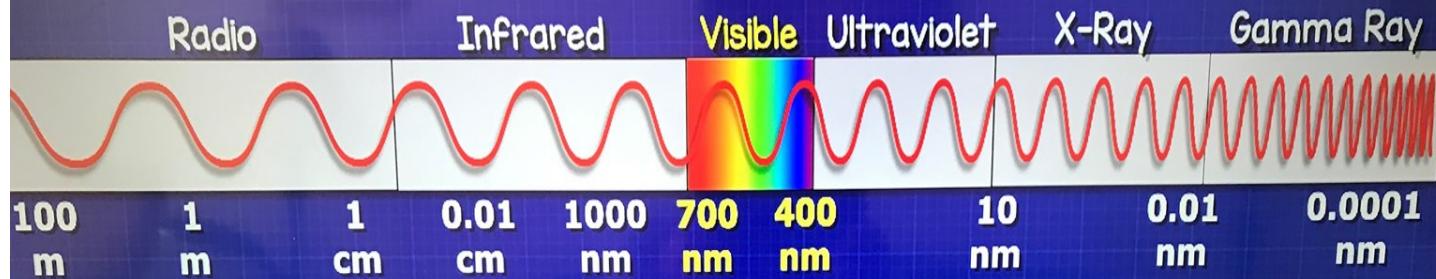

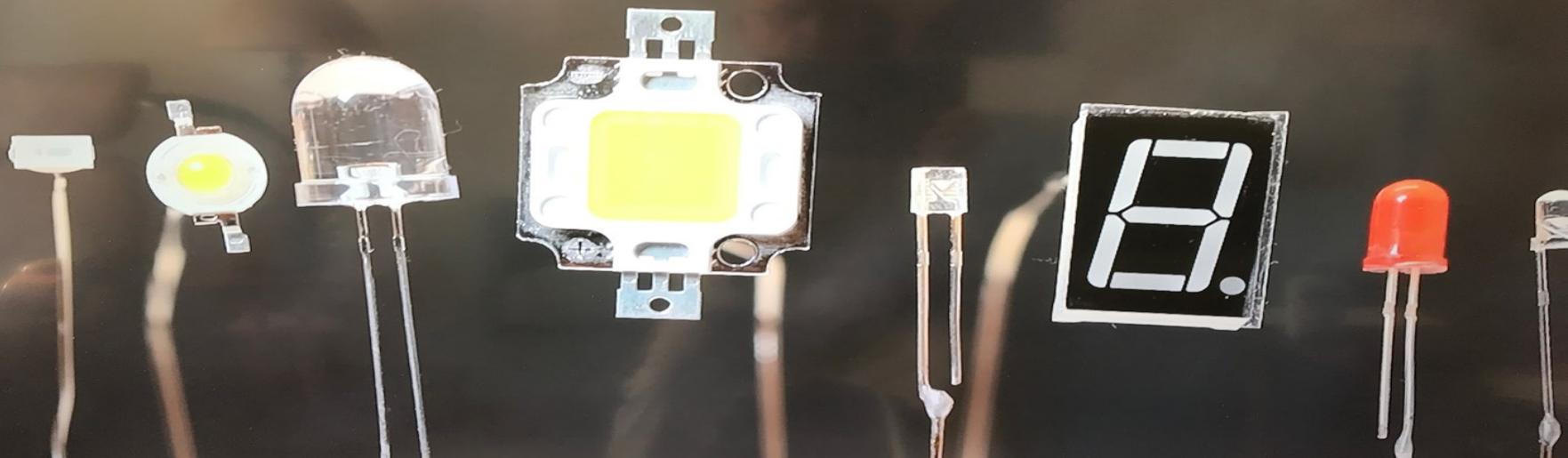

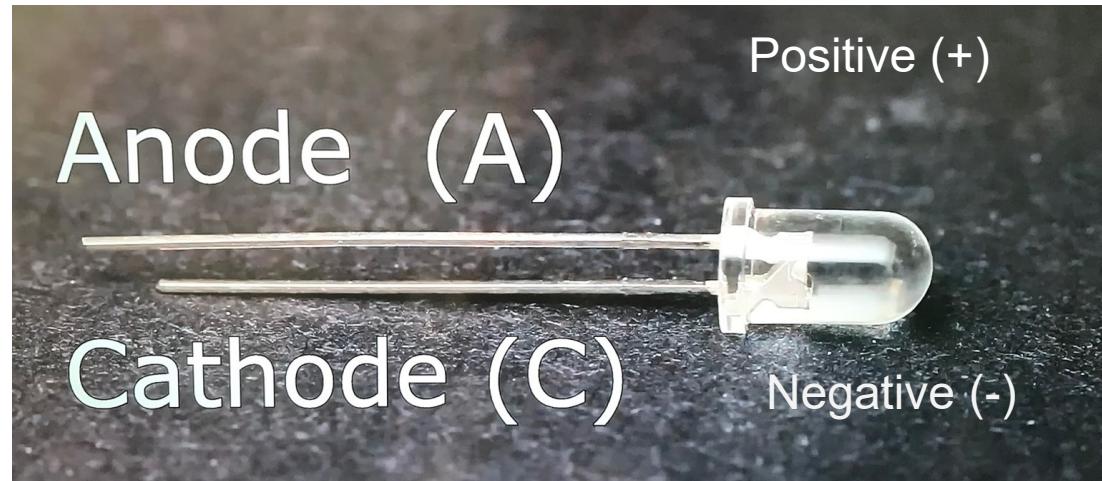

LED Circuit Design






Semiconductor



TheEngineeringMindset.com


TCL

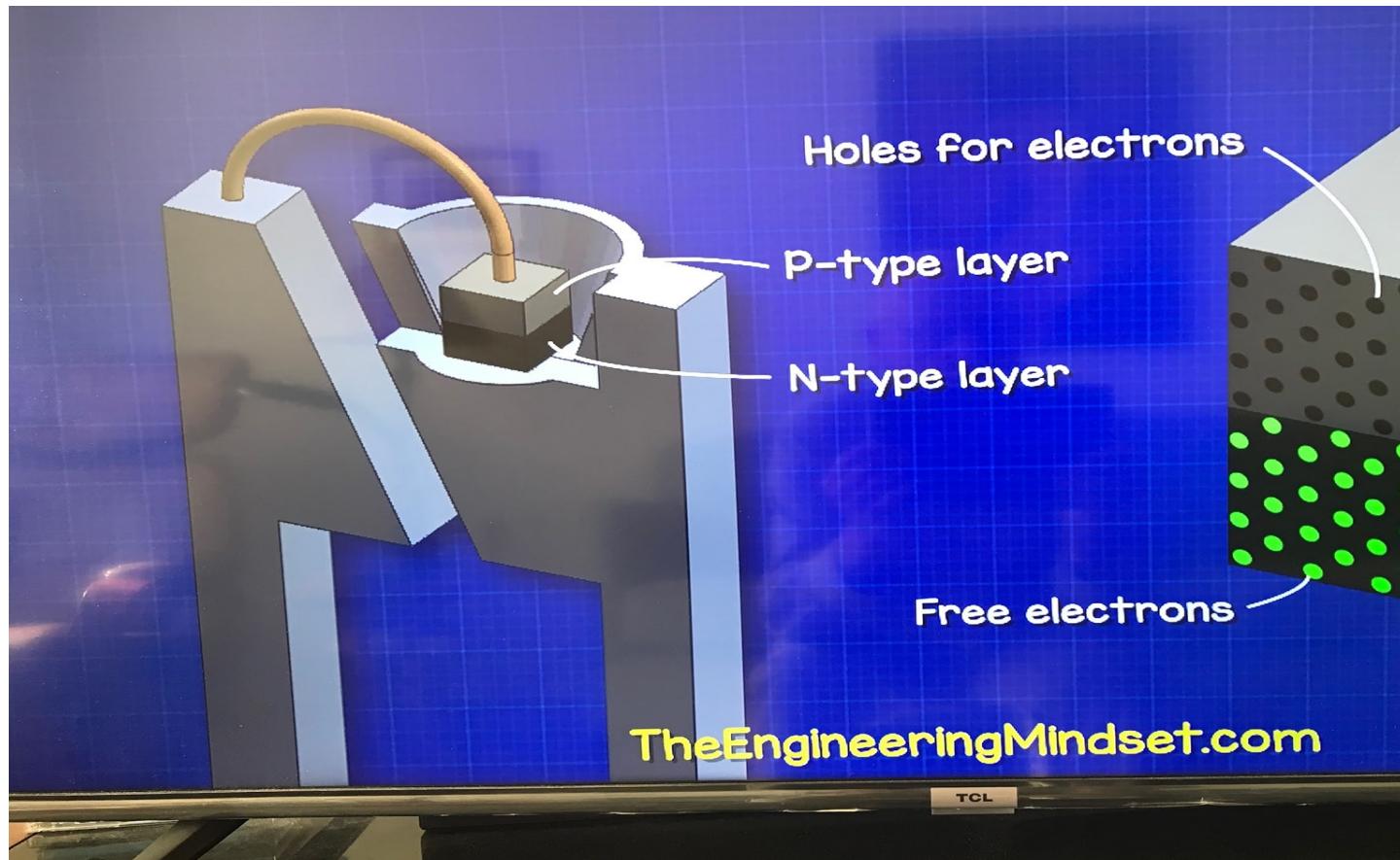




In-video links

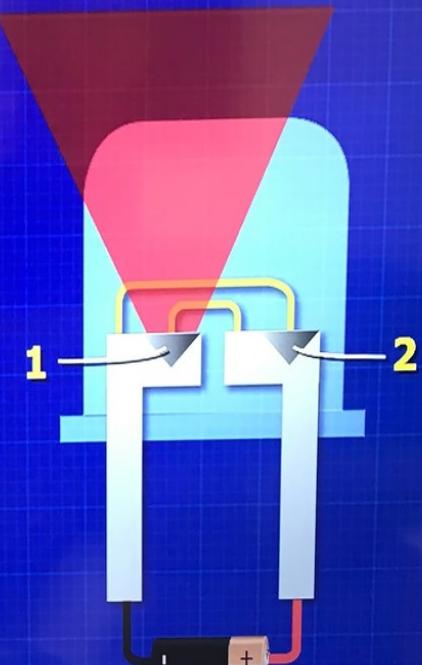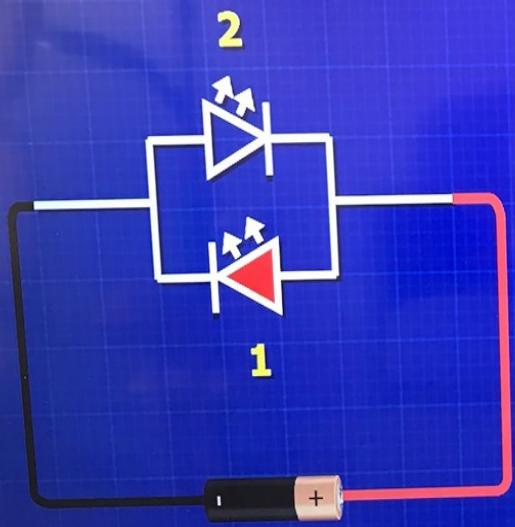


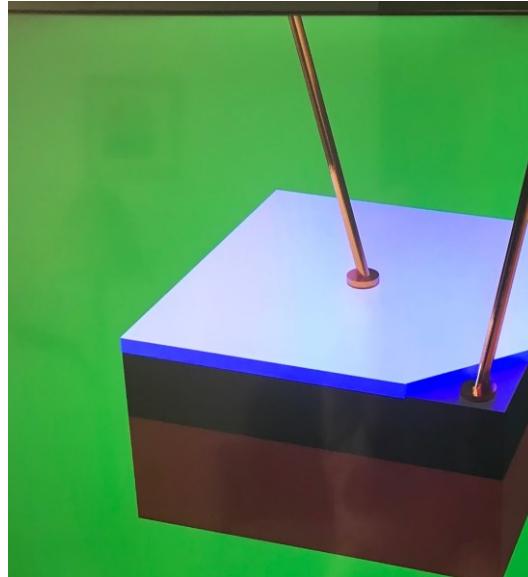

LED Light Bulb

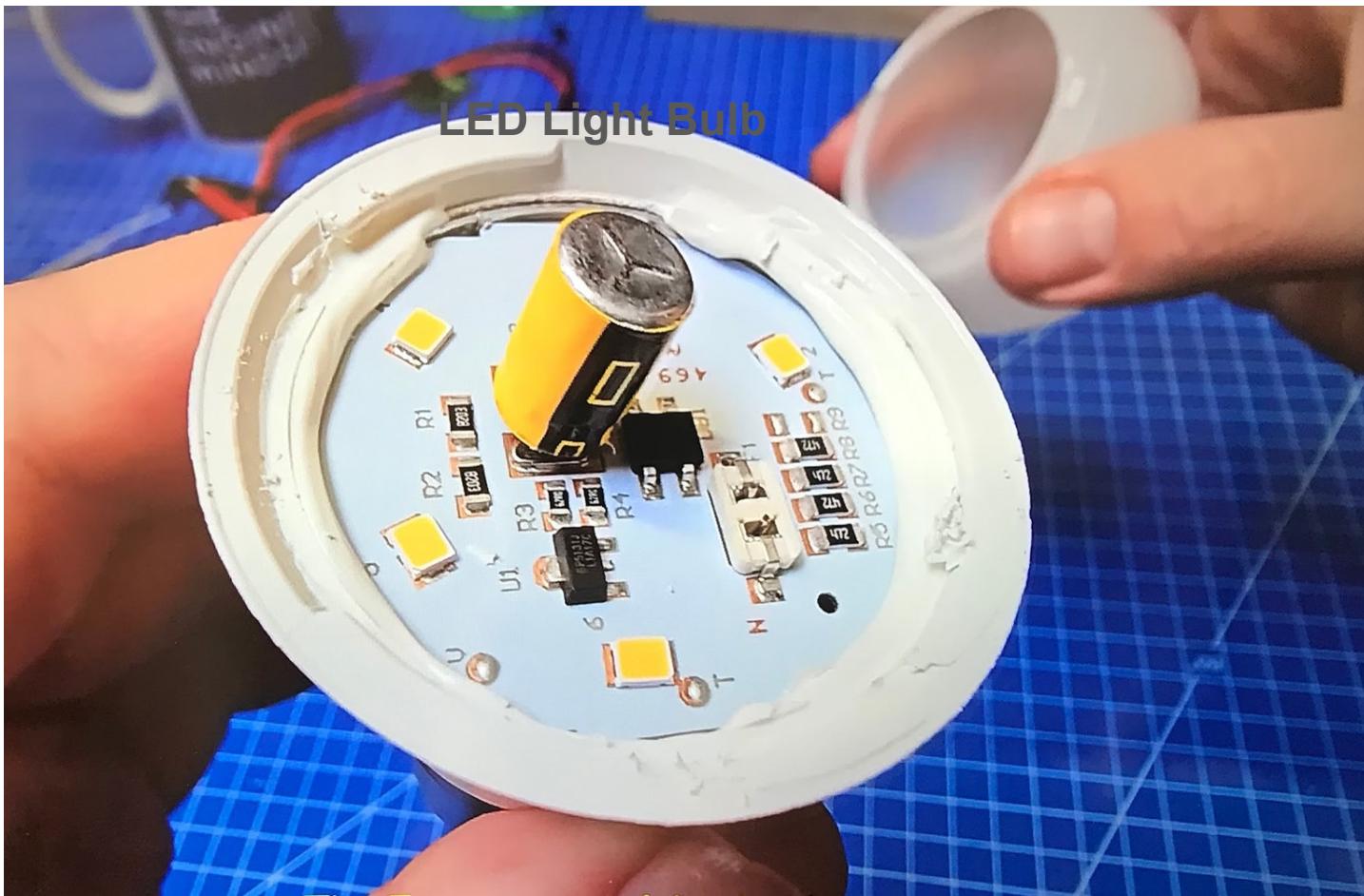

LED Circuit Design

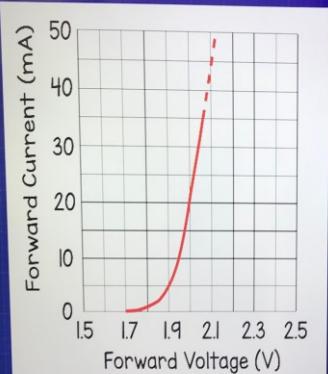

LED Circuit Design

Performance variance is due to:

- Materials used
- Manufacturing process

Try to use LED's from the same batch
and from reliable manufacturers




LED Circuit Design

Color	Forward Voltage @ 20mA
RED	2.0
Orange	2.2
Yellow	2.2
Blue	3.2
Green	3.2

Or use table of typical values

White 3v

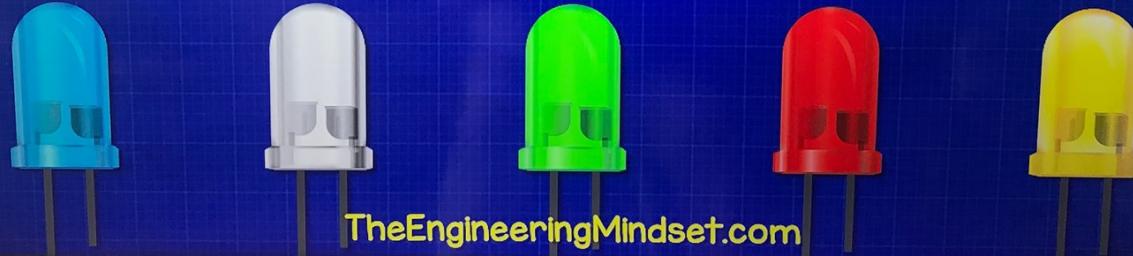

TheEngineeringMindset.com

materials

P-type layer
Semiconductor
N-type layer



GaAsP
Gallium
Arsenide
Phosphide



AlGaP
Aluminium
Gallium
Phosphide



GaAsP:N
Gallium
Arsenide
Phosphide
Nitride



SiC
Silicon
Carbide

TheEngineeringMindset.com

TCL

Ohm's Law

How to Calculate LED Resistance

$$V = RI$$

$$R = V/I$$


$$R =$$

$$\frac{V_{(\text{Supply})} - V_{(\text{LED})}}{I_{(\text{Current})}}$$

(.02 amps)

LED Circuit Design

What size resistor is needed?

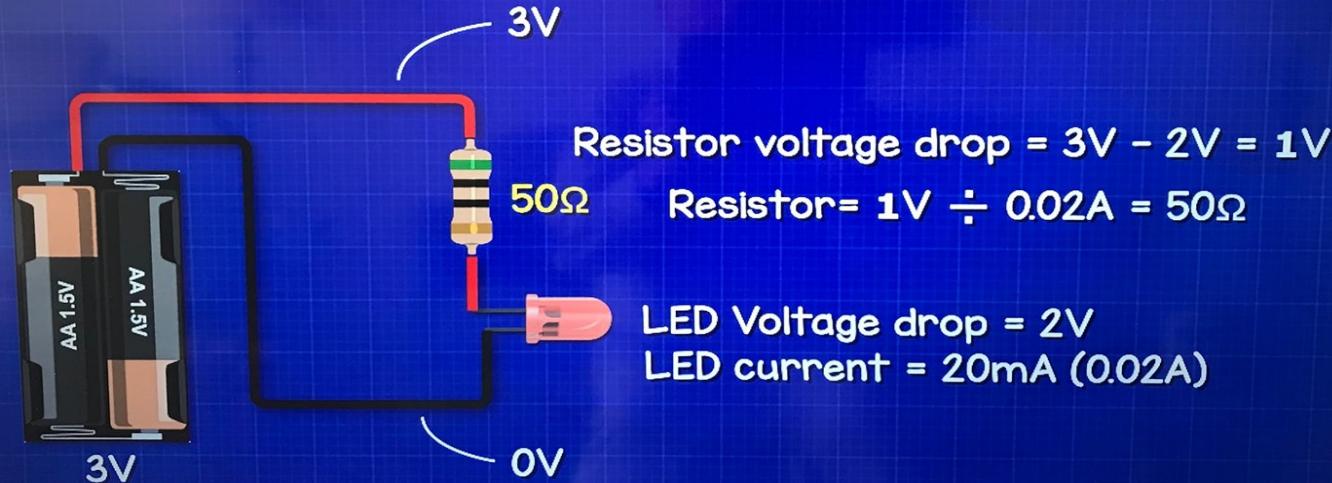

LED Circuit Design



Voltage drop = 2V
Current = 20mA

What size resistor is required?

Resistor voltage drop: $9V - 2V = 7V$

The current required is 20mA

Resistor value = $7V \div 0.02A = 350\Omega$


LED Circuit Design



Calculation:

$$3V - 2V = 1V$$
$$1V \div 0.02A = 50\Omega$$


3V battery
can only power
1 LED at 20mA

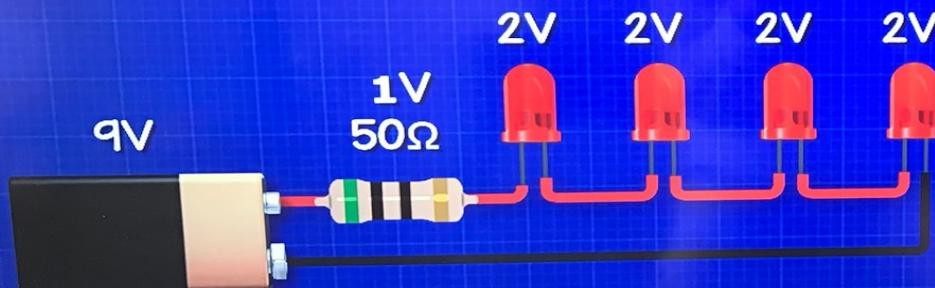

Calculation:

$$9V - 2V - 2V - 2V - 2V = 1V$$
$$1V \div 0.02A = 50\Omega$$

LED Circuit Design

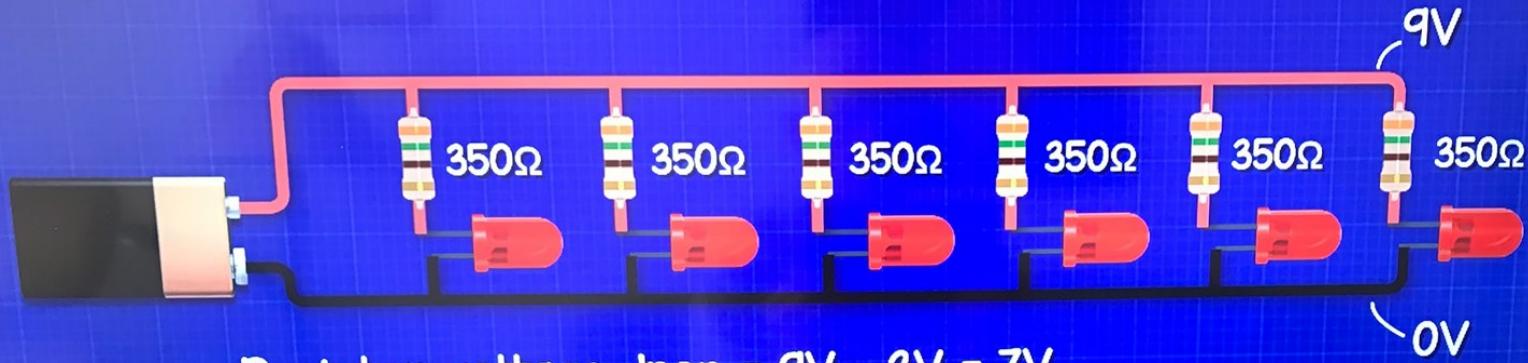

$$\text{Resistor voltage drop} = 9V - 2V = 7V$$


$$\text{Resistor value} = 7V \div 0.02A = 350\Omega$$

$$\text{Resistor power} = 0.02^2 \times 350\Omega = 0.14W$$

$$\text{Total current} = 0.02A \times 6 \text{ LED's} = 0.12A$$

Voltage drop 2V, Current required 20mA

LED Circuit Design

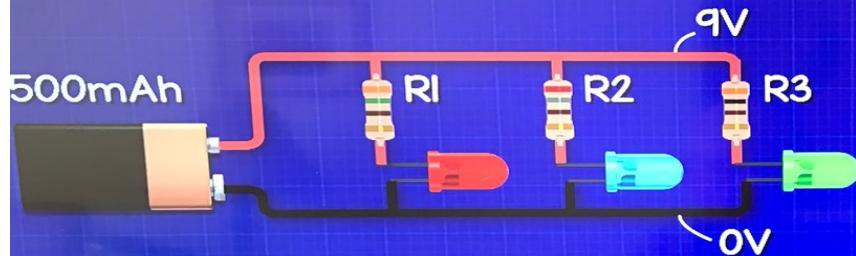

Resistor 1

$$9V - 2V = 7V$$

$$7V \div 0.02A = 350\Omega$$

Resistor 2

$$9V - 3.4V = 5.6V$$

$$5.6V \div 0.02A = 280\Omega$$

Total current = $20mA + 20mA + 20mA = 60mA$

Battery life = $500mAh \div 60mA = \sim 8 \text{ Hours}$

Voltage drop

2V

3.4V

3V

Each requires 20mA

Resistor 3

$$9V - 3V = 6V$$

$$6V \div 0.02A = 300\Omega$$

LED Circuit Design



Voltage drop per branch = $2V + 2V + 2V = 6V$


Resistor voltage drop = $9V - 6V = 3V$

Resistor value = $3V \div 0.02A = 150\Omega$

Current per branch doesn't increase
so we can add more LED's
until maximum voltage drop

Voltage drop 2V, Current required 20mA



<https://evandesigns.com/>

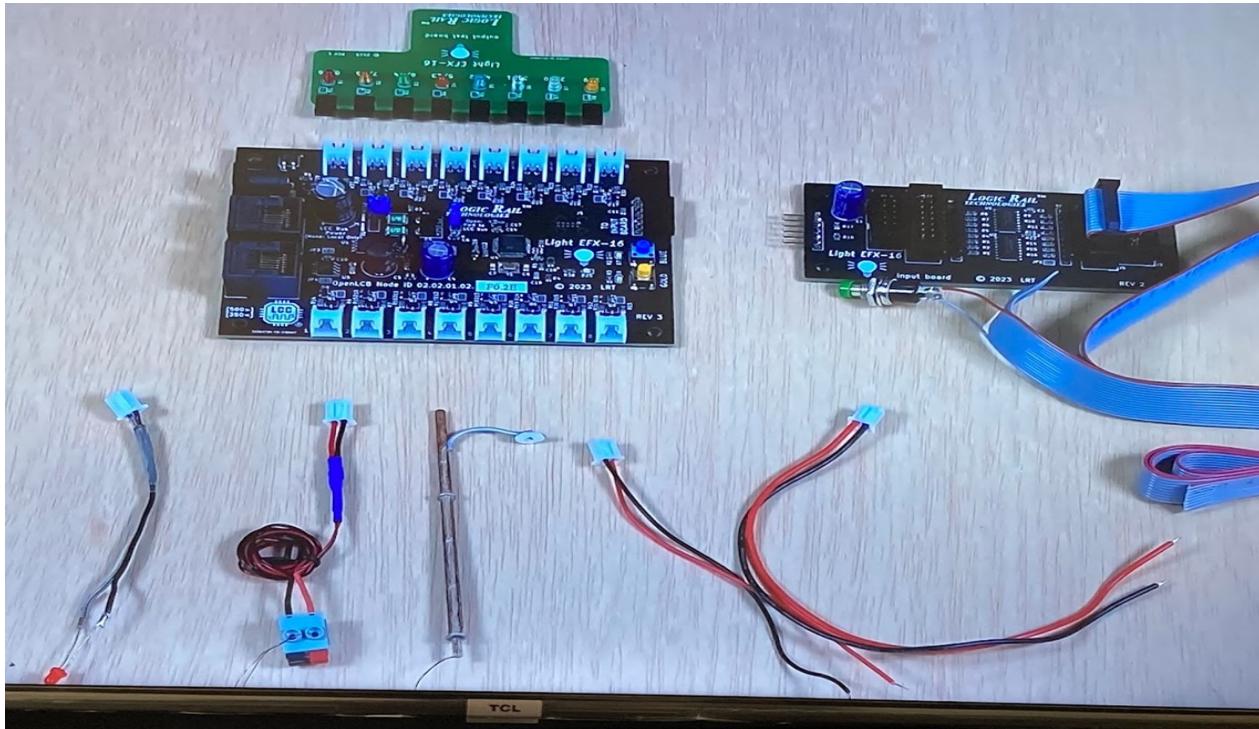

COST \$\$\$\$
Com Board - \$100
Input Bd - \$ 20
Input Cable - \$ 6
Output Cable - \$. 5

System \$200 +
(add light LED cost)

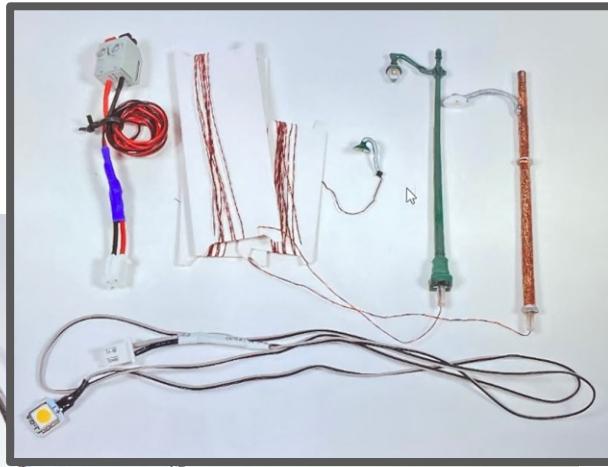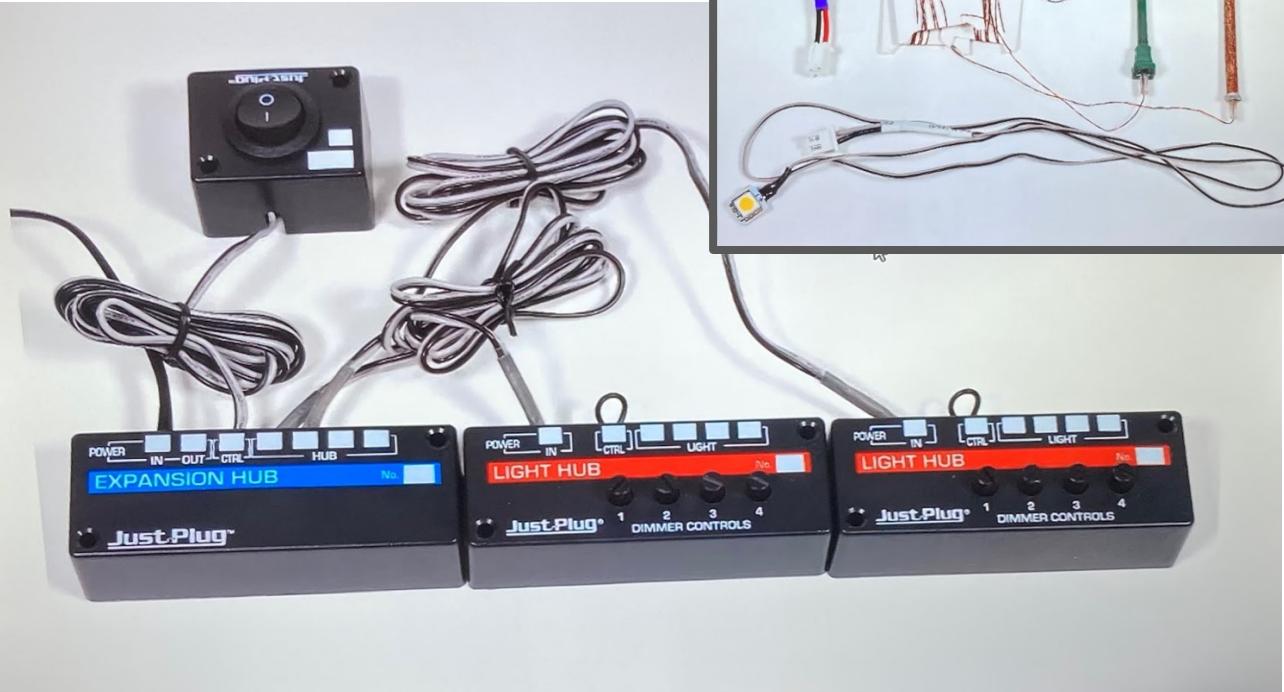Lighting System - Logic Rail Technologies



COST \$\$\$

Light Hub - \$15

Exp Hub - \$14

Pwr Sup - \$20

Ext Cables - \$ 6

Light Switch - \$ 9

System Costs

\$100+

(add LED cost)

Lighting System - Woodland Scenics

Anode (A)




Cathode (C)

The short lead is the cathode (-) Black

The long lead is the anode (+) RED

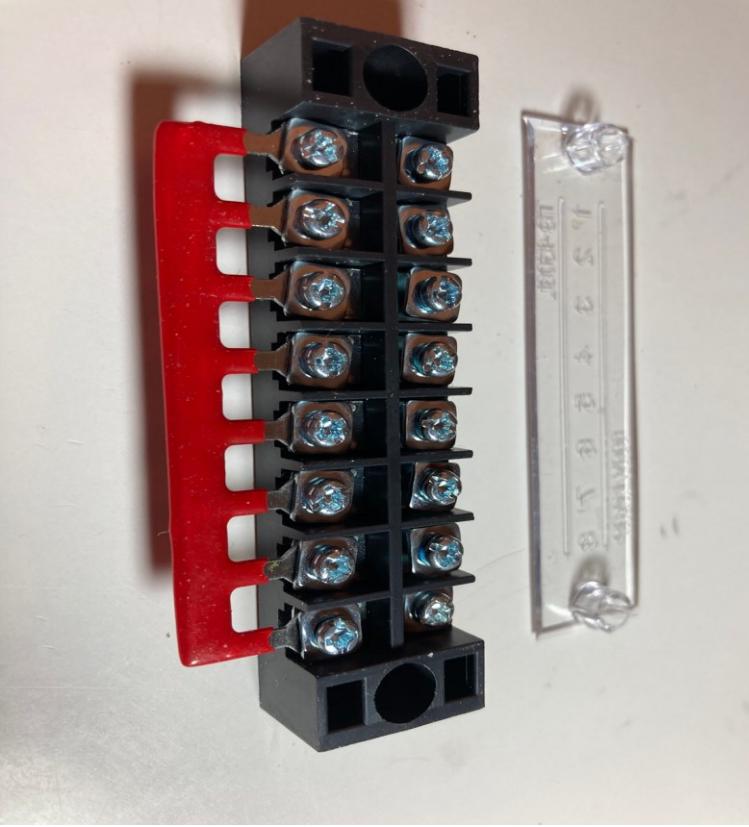If LED has Flat Side: it is the cathode (-)



Type of wiring connectors used on the NWV layout

TYPES OF WIRE



Wire Cost

Magnet Wire - \$12 (800ft)
Twisted Wire - \$ 8 (30ft)
Coiled wire - \$10 (50ft)




LED Tape Cost

JUNWEN reel - \$14.95

Use - 50,000 hrs

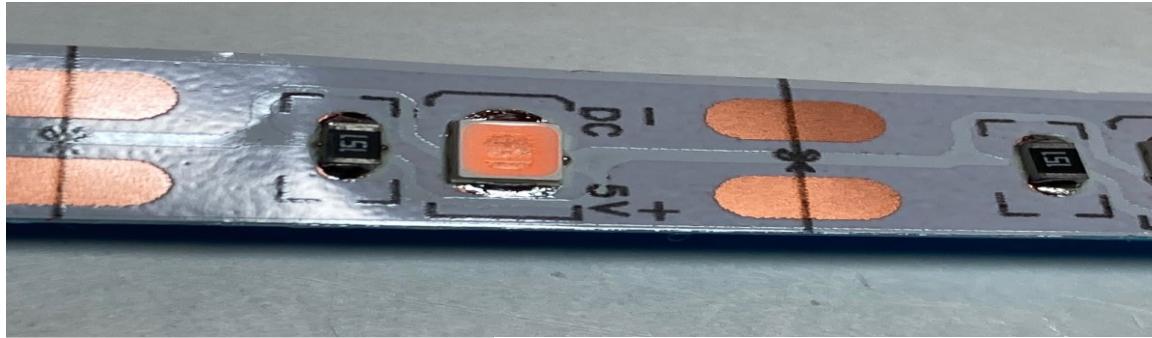Cut - 3 LEDS, 7 LEDS strips/ft, ~142 LEDS/reel
~ \$.11 per LED cut





Lighting Strips with SMDs

Note : positive (+) and negative (-) terminals

- : required forward voltage (don't exceed)
- : attach to models using backing tape plus super glue
- : use RED for anode and BLACK for cathode

Typical LED Lights

